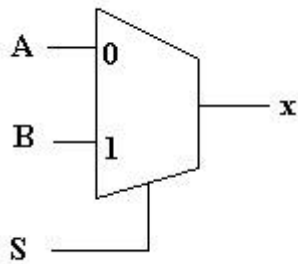



Multiplexer :-

Multiplexer :-

A multiplexer circuit has a number of data inputs, one or more select inputs, and one output. The following figure shows a multiplexer.




S	X
0	A
1	B

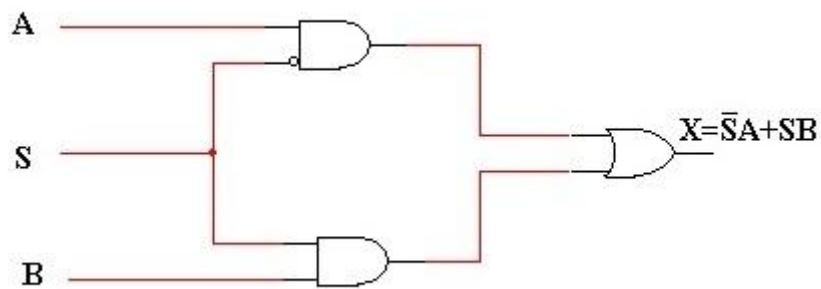


Sum-of-products circuit

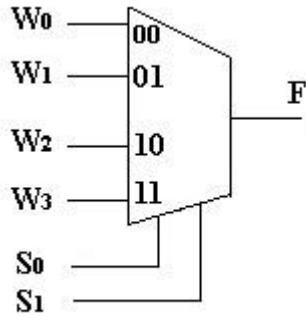A larger multiplexer with four data inputs W_0, W_1, W_2, W_3 and two select inputs, S_1 and S_0 is shown below :-



S_1	S_0	F
0	0	W_0
0	1	W_1
1	0	W_2
1	1	W_3

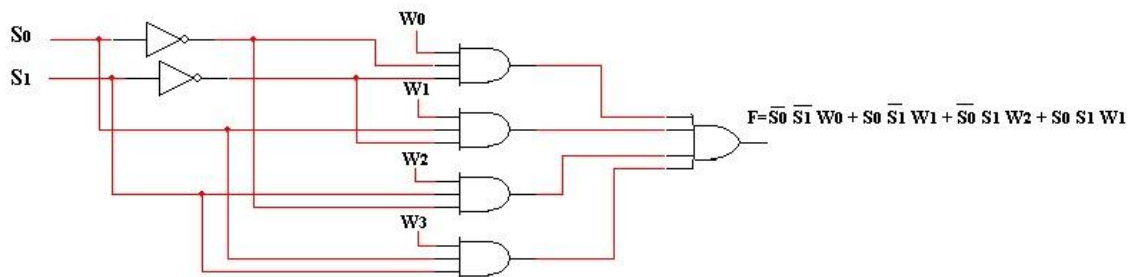


Example:-

Realize 4-to-1 Multiplexer using 2-to-1 Multiplexers .

Solution :-

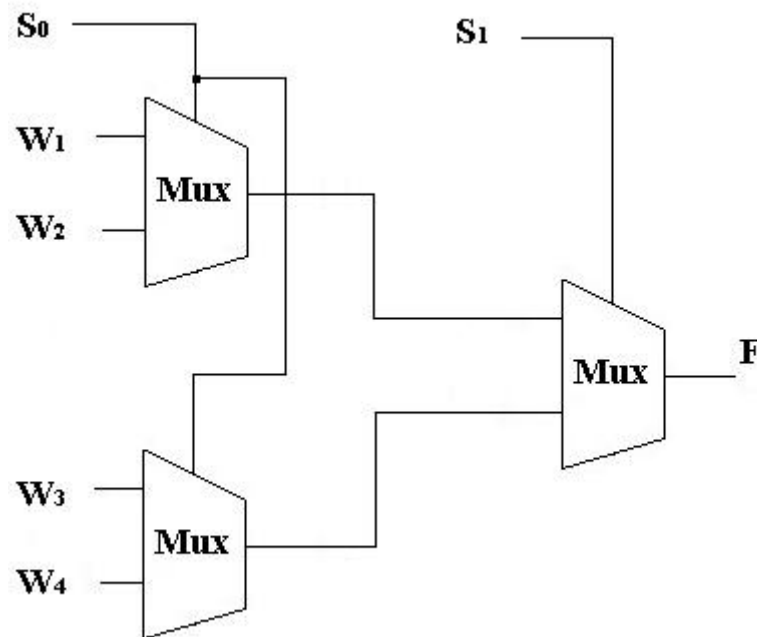A 4-to-1 Multiplexers can be realized using three 2-to-1 Multiplexers as shown below :



H.W :- Realize 16-to-1 Multiplexer using 4-to-1 Multiplexers.


Note:-

- 1) The number of data inputs, n , is an integer power of two.
- 2) A multiplexer that has n data inputs, requires $\lceil \log_2 n \rceil$ select inputs.
- 3) $\log_2 n = \frac{\log_{10} n}{\log_{10} 2}$

Synthesis Of Logic Function Using Multiplexers :-

Consider the example shown below :


W_1	W_2	F
0	0	0
0	1	1
1	0	1
1	1	0

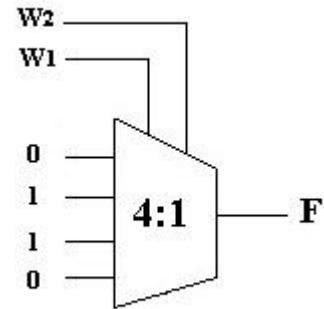

The above implementation is straight forward, but it is not very efficient. A better implementation can be derived as shown below :

W_1	W_2	F
0	0	0
0	1	1
1	0	1
1	1	0

W_1	F
0	W_2
1	$\overline{W_2}$

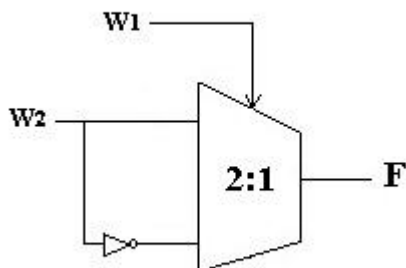


H.W :- Implement three-input XOR using 4-to-1 Multiplexer.

Example :- Realize the following tables using Multiplexers.


1)

W_1	W_2	F
0	0	1
0	1	0
1	0	1
1	1	1

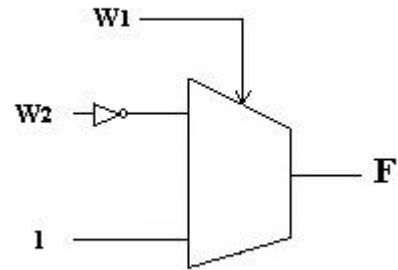

2)


W_1	W_2	W_3	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

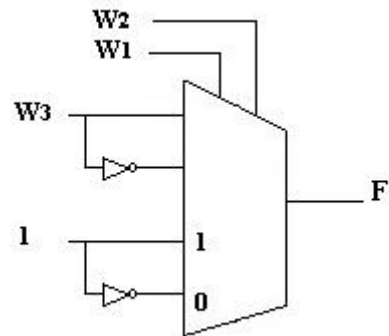


Demultiplexer (Data Distributer) :-

A demultiplexer perform the reverse operation of multiplexer; it takes a single input and distributes it over several outputs.


Example :- (1-line to 4-line Demux)

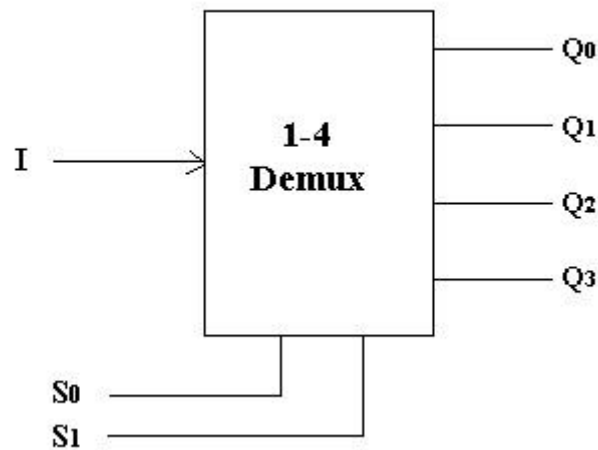


S_1	S_0	Q_0	Q_1	Q_2	Q_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

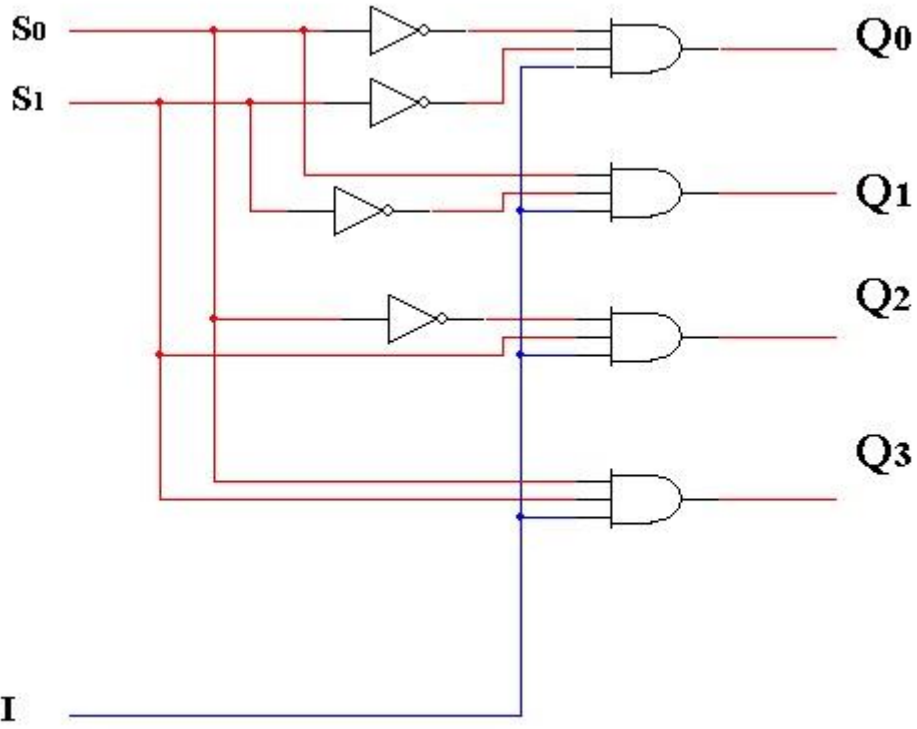

Types of Multiplexer :-

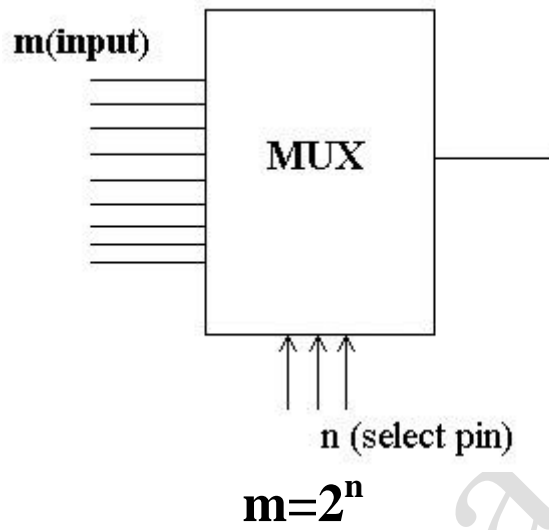

1) (2x1)

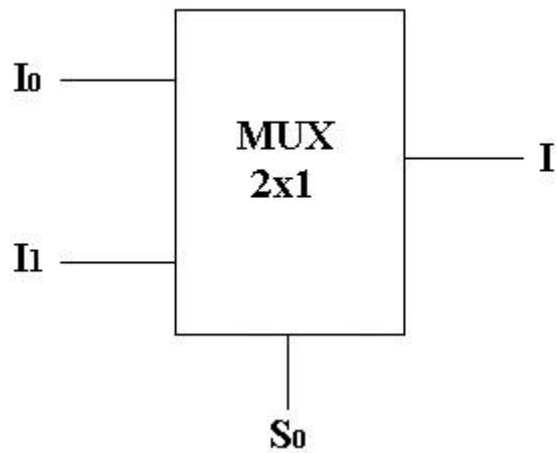


$$2^1=2$$


S_0	F
0	I_0
1	I_1

2) (4x1)

S_1	S_0	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

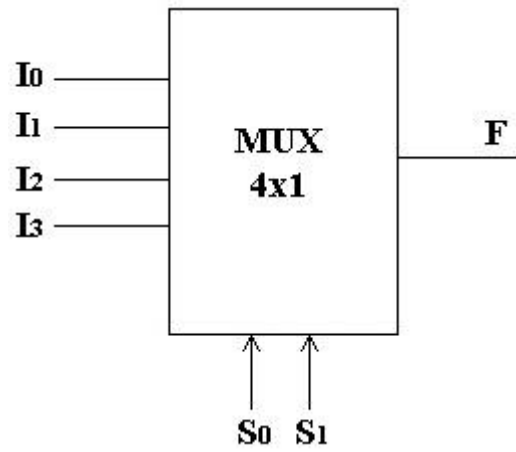
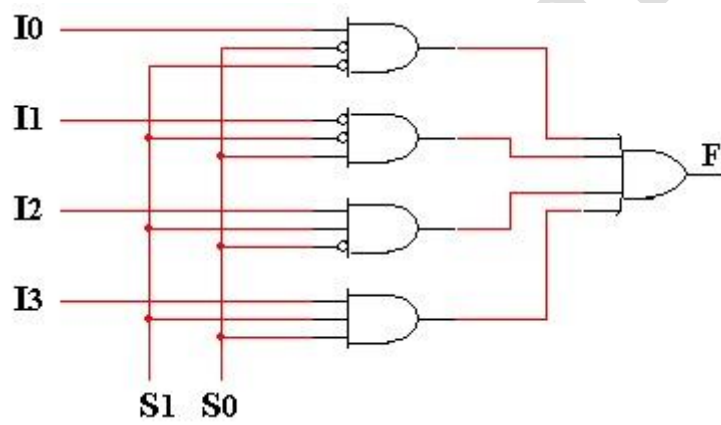
$$F = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$



How To Design Mux By Using Function :-


- 1- Number of select pin equal (no. of variable – 1)
- 2- The most variable in the select pin.
- 3- Put the last variable on input Mux.

Ex:- design Mux using function below.

$$F_{A,B,C} = \sum(0,1,4,7)$$

No. select = 3-1 = 2

∴ Mux = 4x1

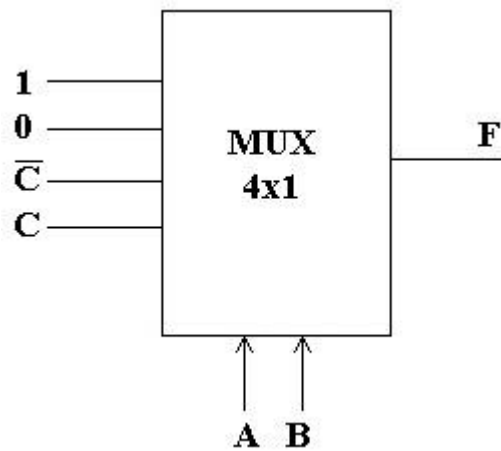

A	B	C	F	
0	0	0	1	$I_0=1$
0	0	1	1	
0	1	0	0	$I_1=0$
0	1	1	0	
1	0	0	1	$I_2 = \bar{C}$
1	0	1	0	
1	1	0	0	$I_3 = C$
1	1	1	1	

Design Using K-map :-


4x1 \implies put A,B in select pin

$I_0=?$

$I_1=?$

$I_2=?$

$I_3=?$

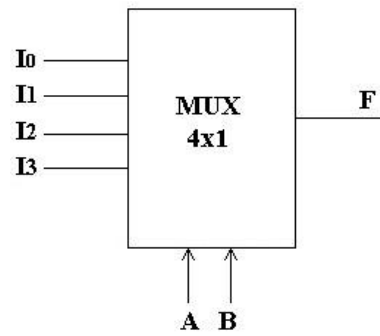

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	I_0	I_0	I_0	I_0
$\bar{A}B$	I_1	I_1	I_1	I_1
AB	I_3	I_3	I_3	I_3
$A\bar{B}$	I_2	I_2	I_2	I_2

8x1 \implies put A,B,C in select pin

$I_0=?$

$I_1=?$

$I_2=?$


$I_3=?$

$I_4=?$

$I_5=?$

$I_6=?$

$I_7=?$

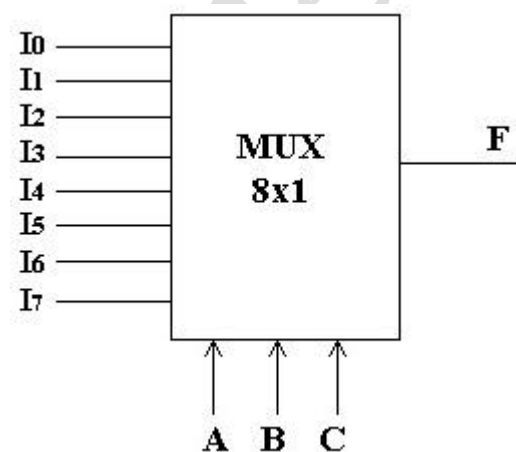

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	I_0	I_0	I_1	I_1
$\bar{A}B$	I_2	I_2	I_3	I_3
AB	I_6	I_6	I_7	I_7
$A\bar{B}$	I_4	I_4	I_5	I_5