

11. Single-phase AC Controller with R-L load

The single –phase AC controller with resistive load is shown in Fig.11.1. Due to the inductance in the circuit , the current in thyristor T1 would not fall to zero at $\omega t = \pi$, when the source voltage v_s start to be negative. Thyristor T1 continues to conduct until its current i_1 falls to zero at $\omega t = \beta$.

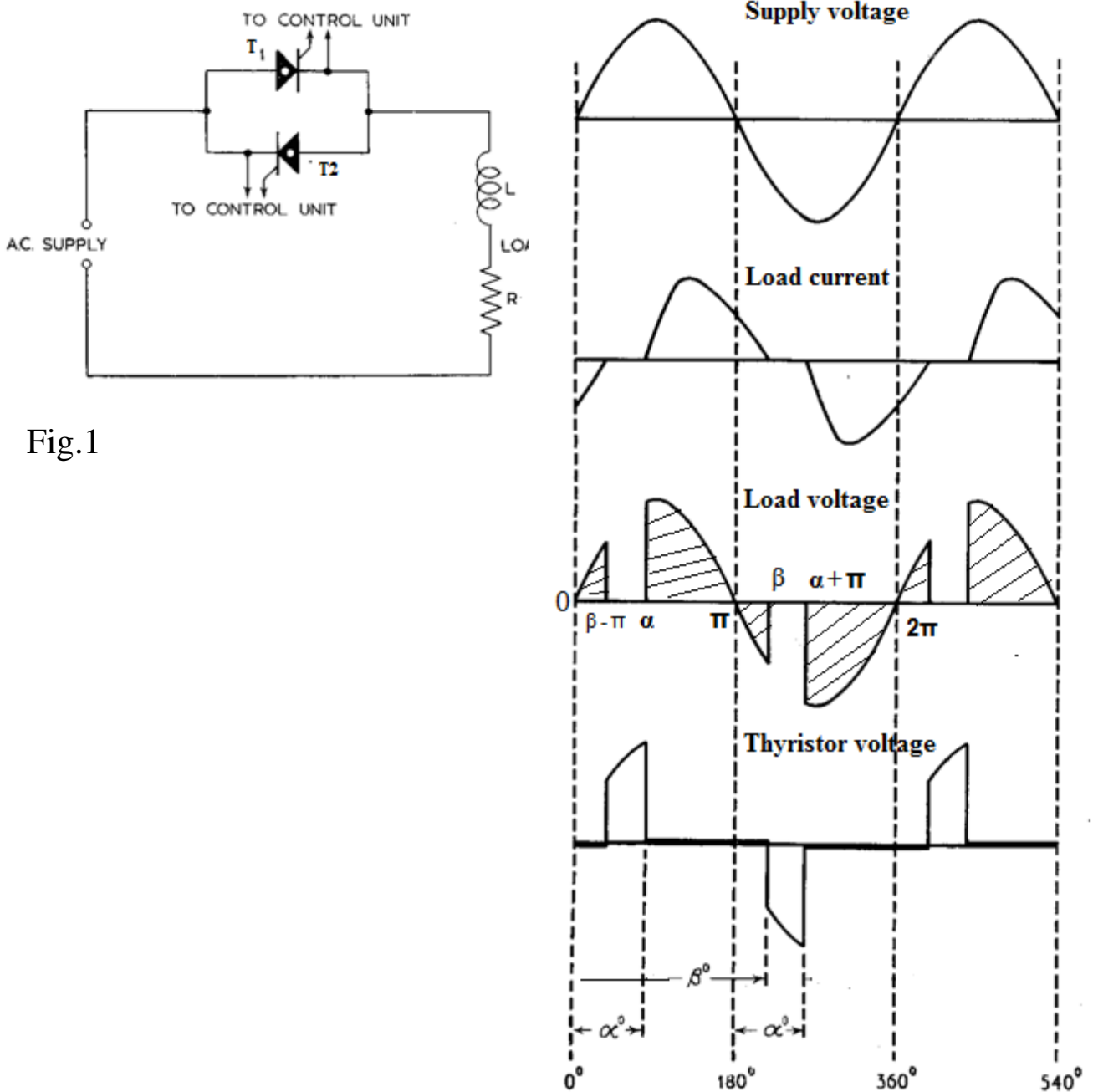


Fig.1

By KVL;

$$v_s = v_o = V_R + v_L$$

The equation for the current through R-L load can be found from the solution of the differential equation:

$$L \frac{di}{dt} + i R = V_m \sin \omega t$$

The solution of this differential equation is:

- The start of conduction is delayed until $\omega t = \alpha$. Subsequent to triggering, let the instantaneous current $i(\omega t)$ consists of hypothetical steady-state components $i_{ss}(\omega t)$ and transient component $i_{trans}(\omega t)$,

$$\therefore i(\omega t) = i_{ss}(\omega t) + i_{trans}(\omega t)$$

Now at $\omega t = \alpha$, the instantaneous steady-state component has the value,

$$i_{ss}(\alpha) = \frac{V_m}{Z} \sin(\alpha - \theta)$$

where

$$Z = \sqrt{R^2 + \omega^2 L^2}$$

$$\theta = \tan^{-1} \frac{\omega L}{R}$$

The transient component of the current,

$$i_{trans} = Ae^{-\frac{R}{L}t}$$

Hence the equation for the current i ,

$$i(\omega t) = \frac{V_m}{Z} \sin(\omega t - \theta) + Ae^{-\frac{R}{L}t} \quad \alpha \leq \omega t \leq \beta$$

The constant A can be found from the initial conditions:

At $\omega t = \alpha$, $i = 0$, hence from eq.(2),

$$A = -\frac{V_m}{Z} \sin(\alpha - \theta) e^{-\left(\frac{R}{L}\right)\left(\frac{\alpha}{\omega}\right)}$$

- Subsequent to α

The transient component decay exponentially from it's instantaneous value of $\left[-\frac{V_m}{Z} \sin(\alpha - \theta)\right]$ by the time constant $\tau = \frac{L}{R}$. Thus


$$i_{trans}(\omega t) = -\frac{V_m}{Z} \sin(\alpha - \theta) e^{-\frac{t}{\tau}}$$

For $\omega t > \alpha$,

$$i_{trans}(\omega t) = -\frac{V_m}{Z} \sin(\alpha - \theta) e^{-\frac{R}{\omega L}(\omega t - \alpha)}$$

- The complete solution for the current at first cycle
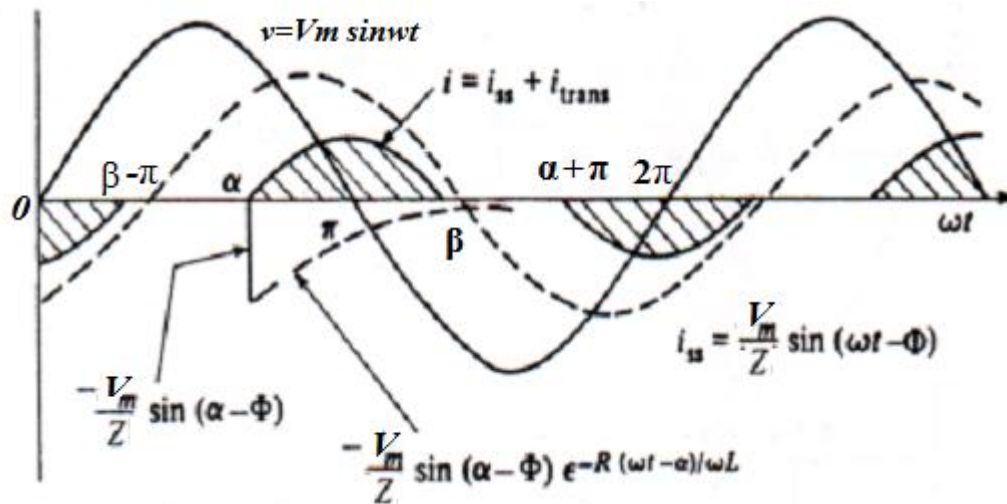
$$i(\omega t) = \frac{V_m}{Z} \sin(\omega t - \theta) - \frac{V_m}{Z} \sin(\alpha - \theta) e^{-\frac{R}{\omega L}(\omega t - \alpha)}$$



Extinction Angle β

For the current in the interval $\alpha \leq \omega t \leq \beta$

$$i(\omega t) = \frac{v_m}{Z} \sin(\omega t - \theta) - \frac{V_m}{Z} \sin(\alpha - \theta) e^{-\frac{R}{\omega L}(\omega t - \alpha)}$$

But at $\omega t = \beta$, $i(\omega t) = 0$, hence

$$0 = \frac{v_m}{Z} \sin(\beta - \theta) - \frac{V_m}{Z} \sin(\alpha - \theta) e^{-\frac{R}{\omega L}(\beta - \alpha)}$$

But $\frac{R}{\omega L} = \cot \theta$

$$\therefore 0 = \sin(\beta - \theta) - \sin(\alpha - \theta) e^{-\cot \theta (\beta - \alpha)}$$

If α and θ are known, β can be calculated. However, this is a transcendental equation (i.e. cannot be solved explicitly and no way of obtaining $\beta = f(\alpha, \theta)$).

Method of solution is by iteration,

e.g. If $\theta = 60^\circ$, $\alpha = 120^\circ = 2\pi / 3$

$$\cot \theta = 0.578$$

$$\sin(\beta - 60^\circ) = \sin(120^\circ - 60^\circ) e^{-0.578(\beta - \frac{2\pi}{3})} \Rightarrow \beta = 222^\circ$$

Approximate solution of β :-

$$\beta = 180^\circ + \theta - \Delta$$

where

$$\begin{aligned} \Delta &= 5^\circ \sim 10^\circ \text{ for large } R \text{ and small } \omega L \\ &= 10^\circ \sim 15^\circ \text{ for } R = \omega L \\ &= 15^\circ \sim 20^\circ \text{ for small } R \text{ and large } \omega L \end{aligned}$$


For the previous example,

$$\begin{aligned} \theta &= 60^\circ, \Delta = 15^\circ - 20^\circ \\ \therefore \beta &= 180^\circ + 60^\circ - 15^\circ = 225^\circ \\ &\text{or} \\ \beta &= 180^\circ + 60^\circ - 20^\circ = 220^\circ \end{aligned}$$

$$\beta = \frac{225 + 220}{2} = 222.5^\circ$$

Load voltage waveform analysis

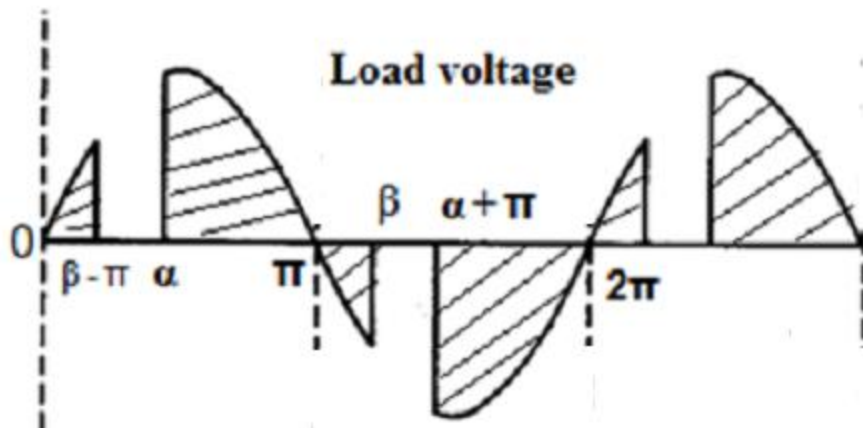The load voltage waveform for R-L load with AC chopper is shown in Fig.



This waveform can be represented as :

$$v_L(\omega t) = V_m \sin \omega t \Big|_{0, \alpha, \pi + \alpha}^{\beta - \pi, \beta, 2\pi}$$

$$= 0 \quad \text{elsewhere}$$

Fourier analysis of the above waveform,

$$a_0 = \frac{1}{\pi} \int_0^{2\pi} v_L(\omega t) d\omega t = 0$$

$$a_1 = \frac{1}{\pi} \int_0^{2\pi} v_L(\omega t) \cos \omega t d\omega t$$

$$b_1 = \frac{1}{\pi} \int_0^{2\pi} V_m \sin \omega t \cos \omega t \, d\omega t$$

$$a_1 = \frac{1}{\pi} \int_0^{\beta-\pi} V_m \sin \omega t \cos \omega t \, d\omega t + \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \cos \omega t \, d\omega t \\ + \frac{1}{\pi} \int_{\alpha+\pi}^{2\pi} V_m \sin \omega t \cos \omega t \, d\omega t$$

Use the trigonometric relation $\sin 2x = 2 \sin x \cos x$

$$a_1 = \frac{V_m}{2\pi} \left[\int_0^{\beta-\pi} \sin 2\omega t \, d\omega t + \int_{\alpha}^{\beta} \sin 2\omega t \, d\omega t + \int_{\alpha+\pi}^{2\pi} \sin \omega t \, d\omega t \right]$$

$$a_1 = \frac{V_m}{4\pi} \left[-\cos 2\omega t \left\{ \frac{\beta-\pi}{0} \right\} - \cos 2\omega t \left\{ \frac{\beta}{\alpha} \right\} - \cos 2\omega t \left\{ \frac{2\pi}{\pi+\alpha} \right\} \right]$$

$$a_1 = \frac{V_m}{2\pi} [\cos 2\alpha - \cos 2\beta]$$

$$b_1 = \frac{1}{\pi} \int_0^{2\pi} v_L(\omega t) \sin \omega t \, d\omega t$$

$$b_1 = \frac{1}{\pi} \int_0^{\beta-\pi} V_m \sin \omega t \sin \omega t \, d\omega t + \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \sin \omega t \, d\omega t \\ + \frac{1}{\pi} \int_{\alpha+\pi}^{2\pi} V_m \sin \omega t \sin \omega t \, d\omega t$$

$$b_1 = \frac{V_m}{2\pi} [2(\beta - \alpha) - \sin 2\beta + \sin 2\alpha]$$

Worked Examples

Example 1: An ideal single-phase voltage source $V_s = V_m \sin \omega t$ supplies to a series R-L load of phase-angle $\theta = 60^\circ$ via a pair of inverse-parallel connected SCRs. The SCR firing angle $\alpha = 120^\circ$. Calculate the current extinction angle β by an approximate method and use iteration to obtain the accurate value.

Solution

(1) By approximate method $\beta \cong \pi + \theta - \Delta$, For $\theta = 60^\circ$
 $\Delta \cong 15^\circ$.
 $\therefore \beta = 180 + 60 - 15 = 225^\circ$.

(2) By the accurate method:

$$\sin(\beta - \theta) = \sin(\alpha - \theta) e^{\frac{(R/L)(\alpha - \beta)}{\omega}}$$

or $\sin(\beta - \theta) = \sin(\alpha - \theta) e^{-\cot \theta (\beta - \alpha)}$

where: $\frac{R}{\omega L} = \cot \theta = \cot 60^\circ = \frac{1}{\tan \theta} = 0.58$.

$$\alpha = 120^\circ = \frac{2\pi}{3} = 2.09 \text{ rad.}$$

$$\sin(\alpha - \theta) = \sin(120 - 60) = \sin 60 = 0.866.$$

Iterative Evaluation of β .

β		$\sin(\beta - 60^\circ)$	$\sin(\alpha - \theta) e^{-\cot \theta (\beta - \alpha)}$
degrees	rad	(LHS)	
220	3.84	0.342	0.314
222	3.87	0.309	0.308

Example 2:

Two SCRs are connected in inverse-parallel for the voltage control of a single-phase series R-L load of phase angle $\theta = 45^\circ$. These are each triggered at a firing-angle $\alpha = 90^\circ$ with reference to their respective anode voltage waveforms. Estimate (do not calculate) the current extinction angle and use this to calculate the load voltage displacement factor.

Solution:

The current extinction angle β is:

$$\beta = \pi + \theta - \Delta$$

$$\text{with } \theta = 45^\circ, \Delta \cong 10^\circ$$

$$\therefore \beta = \pi + 45 - 10 = 180 + 45 - 10 = 215^\circ \text{ or } 3.75 \text{ rad.}$$

$$a_1 = \frac{V_m}{2\pi} (\cos 2\alpha - \cos 2\beta)$$

$$= \frac{V_m}{2\pi} (-1 - 0.342) = \frac{-V_m}{2\pi} (1.342)$$

$$b_1 = \frac{V_m}{2\pi} [2(\beta - \alpha) - \sin 2\beta + \sin 2\alpha]$$

$$= \frac{V_m}{2\pi} [2(3.75 - 1.57) - 0.94 + 0]$$

$$= \frac{V_m}{2\pi} (3.42)$$

$$\psi_1 = \tan^{-1} \frac{a_1}{b_1} = \tan^{-1} (-0.392) = -21.4^\circ$$

$$\text{Displacement Factor} = \cos \psi_1 = \cos 21.4^\circ = 0.93$$